

■—Numerical Inverse Laplace Transform

■—MNA WITH STAMPS

■—Spice

■—MNA Method

MNA Method

Given a linear circuit with n Nodes and m sources, solve the system

$$\mathbf{A} \cdot \mathbf{X} = \mathbf{B}$$

$$\mathbf{A}_{n+m \times n+m} = \begin{bmatrix} G_{n \times n} & C_{n \times m} \\ C_{m \times n} & D_{m \times m} \end{bmatrix}$$

G have the passive elements: the diagonal elements $G(n,n)$ are the sum of the conductance of each element connected to the node n, and the others $G(i,j)$ are the negative conductance of the element connected to the nodes i,j.

C have the voltage sources, where if a voltage source is connected to nodes m, n, then $C(m,n) = \pm 1$, or zero otherwise.

D is the same of B, but with dependent sorces.

X have the node voltages and currents trhough voltage sources.

For b, $b(n) = \text{sum of the currents through the passive elements into the node } n$, and $b(m) = \text{value of the independent voltage sources } m$.

$$\mathbf{x}_{n+m} = \begin{bmatrix} V_{\#N} \\ I_{V\#M} \end{bmatrix}$$

$$\mathbf{B}_{n+m} = \begin{bmatrix} \Sigma (I_X) \\ V_m \end{bmatrix}$$


Example MNA Method

Vb	1	0	40
R1	1	2	2
R2	2	3	9
R3	3	4	8
R4	2	0	10
R5	3	0	4
Is	0	4	1

$$\chi_s := 1$$

Vb	1	0	40
R1	1	2	2
R2	2	3	9
R3	3	4	8
R4	2	0	10
R5	3	0	4
Is	0	4	1

$$\chi := 1$$

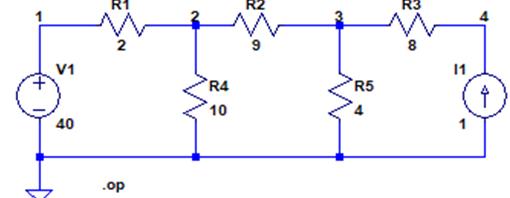

$$G1 := \frac{1}{R1}$$

$$G2 := \frac{1}{R2}$$

$$G3 := \frac{1}{R3}$$

$$G4 := \frac{1}{R4}$$

$$G5 := \frac{1}{R5}$$

$$G := \begin{bmatrix} G1 & -G1 & 0 & 0 \\ -G1 & G1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & G2 & -G2 & 0 \\ 0 & -G2 & G2 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & G3 & -G3 \\ 0 & 0 & -G3 & G3 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & G4 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & -G5 & G5 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & G5 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \quad D := [0]$$

$$C = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad V_b$$

$$B = \begin{bmatrix} 0 \\ 0 \\ 0 \\ -Is \\ Vb \end{bmatrix} \quad \text{at node 4}$$

First V source

$$A = \begin{bmatrix} \frac{1}{R1} & -\frac{1}{R1} & 0 & 0 & 1 \\ -\frac{1}{R1} & \frac{(R2 + R4) \cdot R1 + R2 \cdot R4}{R1 \cdot R2 \cdot R4} & -\frac{1}{R2} & 0 & 0 \\ 0 & -\frac{1}{R2} & \frac{(R3 + R5) \cdot R2 + R3 \cdot R5}{R2 \cdot R3 \cdot R5} & -\frac{1}{R3} & 0 \\ 0 & 0 & -\frac{1}{R3} & \frac{1}{R3} & 0 \\ 1 & 0 & 0 & 0 & 0 \end{bmatrix} \quad B = \begin{bmatrix} 0 \\ 0 \\ 0 \\ Is \\ Vb \end{bmatrix}$$

$$[A \ B \ X \ V \ I] := \text{MNA}("x_s")$$

$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ I_{Vb} \end{bmatrix}$$

Numerically:

$$V = \begin{bmatrix} 40 \\ 30 \\ 12 \\ 20 \\ -5 \end{bmatrix} \quad A^{-1} \cdot B = \begin{bmatrix} 40 \\ 30 \\ 12 \\ 20 \\ -5 \end{bmatrix} \quad \text{Spice} \left["X", ".OP", \begin{bmatrix} "V(1)" \\ "V(2)" \\ "V(3)" \\ "V(4)" \\ "I(Vb)" \end{bmatrix} \right] = \begin{bmatrix} 0 & 40 \\ 0 & 30 \\ 0 & 12 \\ 0 & 20 \\ 0 & -5 \end{bmatrix}$$

Example spice# MNA Method


spice sharp also uses MNA. From:

https://spicesharp.github.io/SpiceSharp/articles/tutorials/writing_behaviors/modified_nodal_analysis.html

$$\begin{pmatrix} \frac{1}{5\Omega} & -\frac{1}{5\Omega} & 0 & 1 \\ -\frac{1}{5\Omega} & \frac{1}{5\Omega} + \frac{1}{10\Omega} + \frac{1}{7\Omega} & -\frac{1}{7\Omega} & 0 \\ 0 & -\frac{1}{7\Omega} & \frac{1}{7\Omega} & 0 \\ 1 & 0 & 0 & 0 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \\ v_3 \\ i_V \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 1.5A \\ 1V \end{pmatrix}$$

$\chi := 1$

V1	1	0	1
R1	1	2	5
R2	2	3	7
R3	2	0	10
I1	0	3	1.5

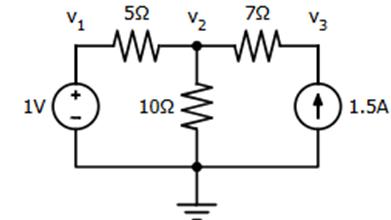

$[A \ B \ X \ V \ I] := \text{MNA} ("X")$

$$A = \begin{bmatrix} 0.2 & -0.2 & 0 & 1 \\ -0.2 & 0.44 & -0.14 & 0 \\ 0 & -0.14 & 0.14 & 0 \\ 1 & 0 & 0 & 0 \end{bmatrix} \quad X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_{V1} \end{bmatrix} \quad B = \begin{bmatrix} 0 \\ 0 \\ 1.5 \\ 1 \end{bmatrix}$$

$$V = \begin{bmatrix} 1 \\ 5.67 \\ 16.17 \end{bmatrix} \quad \text{Spice} \left["X", ".OP", \begin{bmatrix} "V(1)" \\ "V(2)" \\ "V(3)" \\ "I(V1)" \end{bmatrix} \right] = \begin{bmatrix} 0 & 1 \\ 0 & 5.67 \\ 0 & 16.17 \\ 0 & 0.93 \end{bmatrix}$$

□—Ohm's Law


Ohm's Law

$\chi s := 1$

V1	1	0
R1	1	0
R2	1	0

$\chi := 1$

V1	1	0	5
R1	1	0	100
R2	1	0	1k

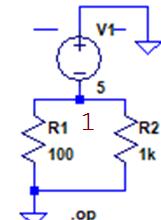

$[A \ B \ X \ V \ I] := \text{MNA} ("xs") \quad V = [V1]$

$$I = \left[-\frac{(R1 + R2) \cdot V1}{R1 \cdot R2} \right]$$

$[A \ B \ X \ V \ I] := \text{MNA} ("X") \quad V = [5]$

$$I = [-0.06]$$


$\text{Spice} ("X", ".OP", "I(V1)") = [0 -0.06]$

$\chi s := 1$

V1	1	2
R1	1	0
R2	2	0

$\chi := 1$

V1	1	2	5
R1	1	0	100
R2	2	0	1k

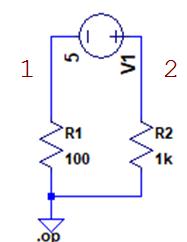

$[A \ B \ X \ V \ I] := \text{MNA} ("xs")$

$$V = \begin{bmatrix} \frac{R1 \cdot V1}{R1 + R2} \\ -\frac{R2 \cdot V1}{R1 + R2} \end{bmatrix} \quad I = \left[-\frac{V1}{R1 + R2} \right]$$

$[A \ B \ X \ V \ I] := \text{MNA} ("X")$

$$V = \begin{bmatrix} 0.45 \\ -4.55 \end{bmatrix}$$

$\text{Spice} ("X", ".OP", \begin{bmatrix} "V(1)" \\ "V(2)" \\ "I(V1)" \end{bmatrix}) = \begin{bmatrix} 0 & 0.45 \\ 0 & -4.55 \\ 0 & 0 \end{bmatrix}$

Note for commercial use
2 / 9

■ Resistive networks

Resistive networks

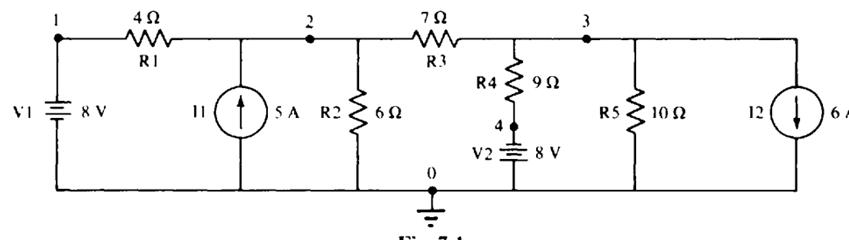


Fig. 7-1

V1	1	0	8
R1	1	2	4
I1	0	2	5
R2	2	0	6
R3	2	3	7
R4	3	4	9
V2	0	4	8
R5	3	0	10
I2	3	0	6

$\chi := 1$

$[A \ B \ X \ V \ I] := MNA("x")$

$$V = \begin{bmatrix} 8 \\ 8.41 \\ -16.07 \\ -8 \end{bmatrix}$$

$$I = \begin{bmatrix} 0.1 \\ 0.9 \end{bmatrix}$$

$$Spice \left["x", ".OP", \begin{bmatrix} "V(1)" \\ "V(2)" \\ "V(3)" \\ "V(4)" \\ "I(V1)" \\ "I(V2)" \end{bmatrix} \right] = \begin{bmatrix} 0 & 8 \\ 0 & 8.41 \\ 0 & -16.07 \\ 0 & -8 \\ 0 & 0.1 \\ 0 & 0.9 \end{bmatrix}$$

■ RL Circuit

RL Circuit

Symbolic and Numerical analysis

V1	1	0
R1	1	2
L1	2	0

$\chi s := 1$

V1	1	0	5
R1	1	2	300
L1	2	0	100

$\chi := 1$

$[A \ B \ X \ V \ I] := MNA("xs")$


$I = \left[-\frac{V1}{R1 + s \cdot L1} \right]$

$V = \left[\frac{V1 \cdot s \cdot L1}{R1 + s \cdot L1} \right]$



$[A \ B \ X \ V \ I] := MNA("x")$

$O := \begin{bmatrix} ".IC V(2) = 0" \\ ".TRAN 0 2 0.1" \end{bmatrix}$

$".IC I(L1) = 0"$

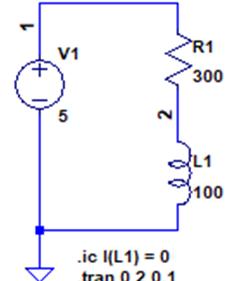

?

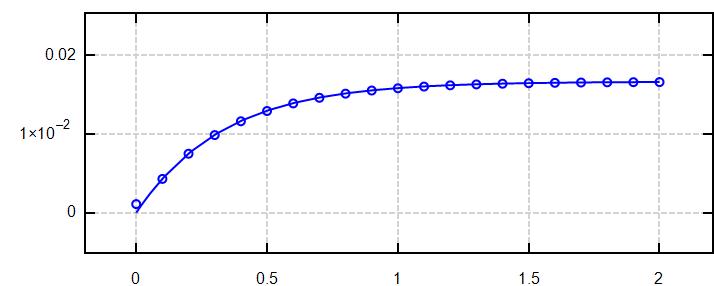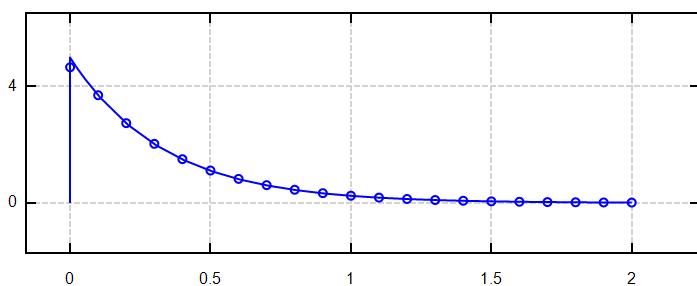

$$\left\{ \begin{array}{l} Spice("x", o, "V(2)") \\ \mathcal{F}\mathcal{L}\left(\frac{V_2}{s}, [0, 0.1 \dots 2]\right) \end{array} \right.$$

$$\left\{ \begin{array}{l} Spice("x", o, "I(L1)") \\ \mathcal{F}\mathcal{L}\left(-\frac{I_1}{s}, [0, 0.1 \dots 2]\right) \end{array} \right.$$

■ RC Circuit

RL Circuit

Symbolic and Numerical analysis


V1	1	0
R1	1	2
C1	2	0

$\chi s := 1$



V1	1	0	12
R1	1	2	22k
C1	2	0	0.9m

$\chi := 1$

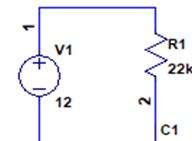X 0.9m is wrong, it correct expression is 900u or 900μ



$\text{Circ}_{A B X V I} := \text{MNA}(\text{"Xs"})$ $I = \left[-\frac{f_{sr.C1}.v1}{1 + s \cdot C1 \cdot R1} \right]$ $V \in \text{versi}[\text{on } V1 \circ f]$ $S \text{ Ma t h}$ $S \text{ t u d i o}$
 $\text{Circ}_{A B X V I} := \text{MNA}(\text{"X"})$ $O := \left[\begin{array}{l} \text{".IC } V(2) = 0 \\ \text{".TRAN } 0 \ 140 \ 0.5 \end{array} \right]$ $.ic V(2) = 0$
 $.tran 0 140 0.5 \text{ startup}$

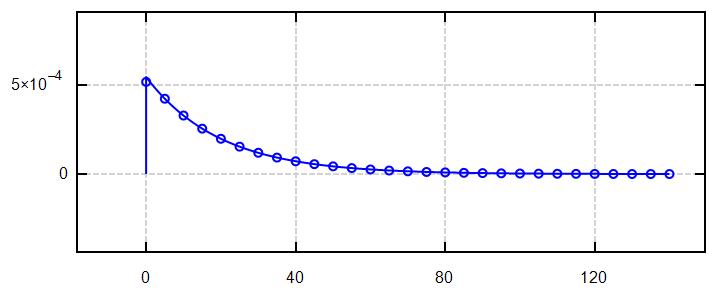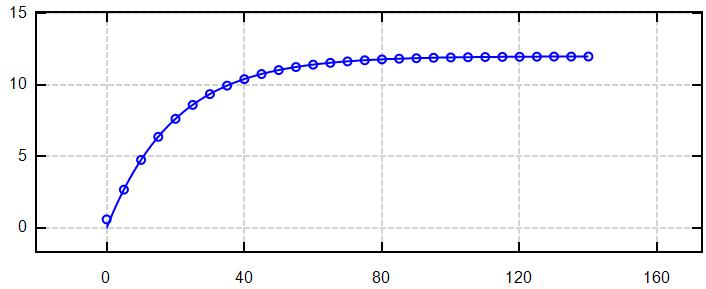

$$\left| \begin{array}{l} \text{Spice}(\text{"X"}, O, \text{"V(2)"}) \\ \text{fz}\left(\frac{v_2}{s}, [0, 5..140]\right) \end{array} \right.$$


$$\left| \begin{array}{l} \text{Spice}(\text{"X"}, O, \text{"I(C1)"}) \\ \text{fz}\left(-\frac{i_1}{s}, [0, 5..140]\right) \end{array} \right.$$

□—opamps

Summary of basic op amp circuits

Shorthand:
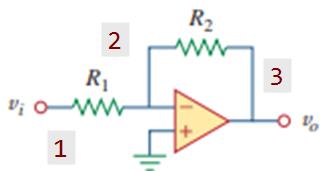
$$V(n) := \boxed{\text{MNA}(\text{"X"})}_n$$




Inverter
amplifier

V.i	1	0
R.1	1	2
R.2	2	3
O	0	3

$$\chi := 1$$
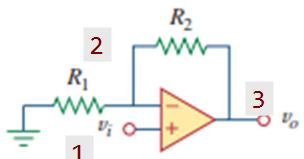
$$V_o := V(3) = -\frac{V_i \cdot R_2}{R_1}$$




Non-
inverter
amplifier

V.i	1	0
R.1	0	2
R.2	2	3
O	1	3

$$\chi := 1$$
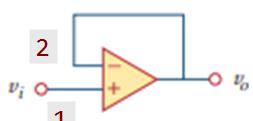
$$V_o := V(3) = \frac{(R_1 + R_2) \cdot V_i}{R_1}$$




Voltage
Follower

V	1	0	V.i
O	1	2	2

$$\chi := 1$$

$$V_o := V(2) = V_i$$

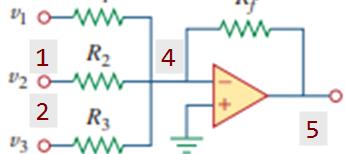

Summer


V	1	0	V.1
V	2	0	V.2
V	3	0	V.3
R	1	4	R.1
R	2	4	R.2
R	3	4	R.3
R	4	5	R.f
O	0	5	4

$$\chi := 1$$

$$V_o := V(5) = -\frac{R_f \cdot ((V_1 \cdot R_2 + V_2 \cdot R_1) \cdot R_3 + V_3 \cdot R_2 \cdot R_1)}{R_3 \cdot R_2 \cdot R_1}$$

or
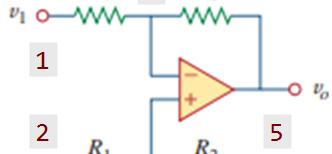
$$V_o = -\left(\frac{R_f}{V_1} + \frac{R_f}{V_2} + \frac{R_f}{V_3} \right)$$



Difference
Amplifier

V	1	0	V.1
V	2	0	V.2
R	1	3	R.1
R	2	4	R.2
R	3	4	R.3
R	4	5	R.f
O	0	5	4

$$\chi := 1$$

$$V_o := V(5) = -\frac{R_f \cdot (V_1 \cdot R_2 + (R_1 + R_3) \cdot V_2)}{(R_1 + R_3) \cdot R_2}$$

or

$$V_o = \frac{R_2}{R_1} \cdot (V_2 - V_1)$$

Note for commercial use

Opamp for spice#


```
.subckt opamp 1 2 3
G1 0 2 1 3 100k
R3 2 0 1
C3 2 0 0.001591549430919
.ends opamp
```

opamp := 1

$$Aol := 100 \cdot E(3) \quad GBW := 10 \cdot E(6)$$

$$\frac{Aol}{2 \cdot \pi \cdot GBW} = 0.001591549430919$$

opamp := description(opamp)

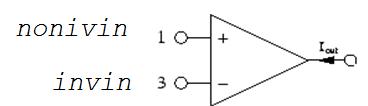

Example with
spice#: Inverter
amplifier

```
V.i 1 0 5
R.1 1 2 10
R.2 2 3 20
X1 0 3 2 opamp
```

$$V_3 = -\frac{V_i \cdot R_2}{R_1}$$

$$Spice \begin{bmatrix} "V(1)" \\ "X" \\ "V(2)" \\ "opamp" \\ "V(3)" \end{bmatrix} = \begin{bmatrix} 0 & 5 \\ 0 & 0 \\ 0 & -10 \end{bmatrix}$$


Sweep analysis

$$\chi := 1$$

$$V_o(R_f) := V(5)$$

$$V_o := -10 \text{ V}$$
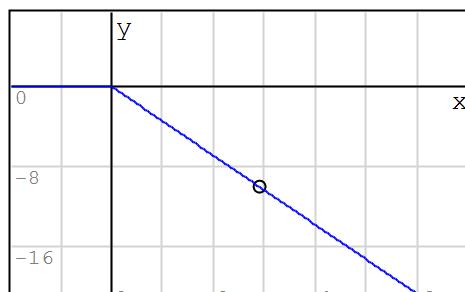
$$R_f := \text{roots}(V_o(R_f) = V_o, R_f) \Omega = 2.9 \Omega$$



$$\begin{cases} V_o(x \Omega) \cdot (x > 0) \\ \text{augment}(R_f, V_o, "o") \end{cases}$$

Sanity check

$$V := \begin{bmatrix} 5 \\ 3 \\ 4 \end{bmatrix} \text{ V} \quad R := \begin{bmatrix} 2 \\ 8 \\ 7 \end{bmatrix} \Omega$$

$$R_f := -\frac{V_o}{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}} = 2.9 \Omega$$


TODO: Sweep analysis with spice#

■—opamp: Capacitance multiplier

Capacitance multiplier

```
Vb 1 0
R1 1 3 1k
R2 1 2 100k
C1 2 0 100n
O1 2 3 3
```

$$[A \ B \ X \ V \ I] := MNA("X")$$

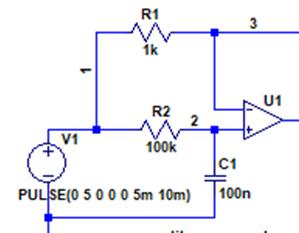

Laplace transform
of a pulse:



$$To := 5 \cdot 10^{-3} \quad Vb := \frac{5}{s \cdot (1 + e^{-To \cdot s})}$$

```
Vb 1 0 PULSE(0 5 0 0 0 5m 10m)
R1 1 3 1k
R2 1 2 100k
C1 2 0 100n
X1 2 3 3 opamp
```

$$O := \begin{bmatrix} opamp \\ ".TRAN 0 0.05 0.1m" \end{bmatrix}$$

$$T := [0, 0.001 \dots 0.05] \quad \text{rows}(T) = 51$$

$$\chi := 1$$

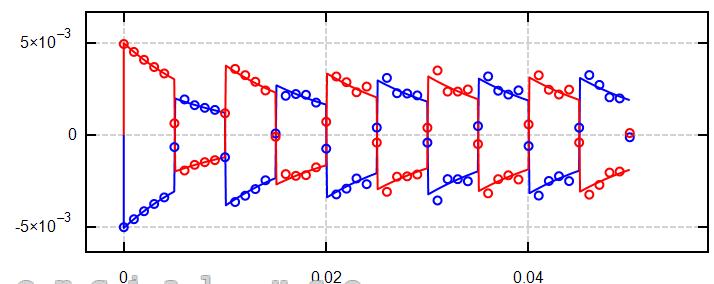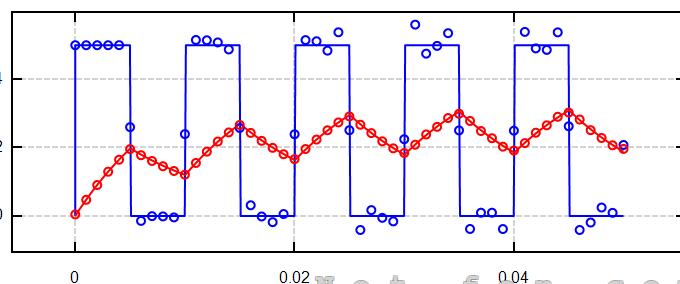

```

Spice("x", 0, "V(1)")
Spice("x", 0, "V(2)")
FL(v1, T)
FL(v2, T)

```

```

Spice("x", 0, "I(Vb)")
Spice("x", 0, "I(R1)")
FL(I1, T)
FL(I2, T)

```

Clear(Vb) = 1

— opamp: DC OP Point —


DC OP Point

Vb	1	0
R1	2	3
R2	3	4
R3	1	2
R4	5	0
C1	2	3
C2	4	5
O1	0	2
O2	0	4

Vb	1	0	12
R1	2	3	1k
R2	3	4	100k
R3	1	2	100k
R4	5	0	100k
C1	2	3	10n
C2	4	5	10n
X1	0	2	3 opamp
X2	0	4	5 opamp

$\chi_s := 1$

$\chi := 1$

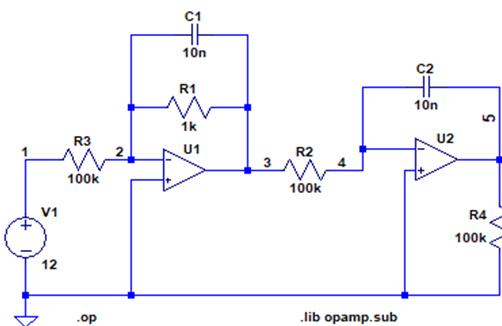

$$[R1 \ R2 \ R3 \ R4] := \left[\frac{1}{G1} \ \frac{1}{G2} \ \frac{1}{G3} \ \frac{1}{G4} \right]$$

$$[A \ B \ X] := MNA("Xs", "ABX", \Sigma)$$

$$A \cdot X = B$$

$$A = \begin{bmatrix} G3 & -G3 & 0 & 0 & 0 & 1 & 0 & 0 \\ -G3 & G3 + G1 + s \cdot C1 & -(G1 + s \cdot C1) & 0 & 0 & 0 & 1 & 0 \\ 0 & -(G1 + s \cdot C1) & G2 + G1 + s \cdot C1 & -G2 & 0 & 0 & 0 & 0 \\ 0 & 0 & -G2 & G2 + s \cdot C2 & -s \cdot C2 & 0 & 0 & 1 \\ 0 & 0 & 0 & -s \cdot C2 & G4 + s \cdot C2 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \end{bmatrix} \quad X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ I_{Vb} \\ I_O1 \\ I_O2 \end{bmatrix} \quad B = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ Vb \\ 0 \\ 0 \end{bmatrix}$$

DC Operating point (C as open circuits):

?

From ltspice:

$$Spice \left("x", \left[".OP" \right], \left["opamp" \right], \left[\begin{array}{c} "V(1)" \\ "V(2)" \\ "V(3)" \\ "I(R4)" \\ "I(Vb)" \end{array} \right] \right) = \begin{bmatrix} 0 & 12 \\ 0 & 1.21 \cdot 10^{-9} \\ 0 & 1.2 \cdot 10^{-9} \\ 0 & 0 \\ 0 & 0 \end{bmatrix}$$

--- Operating Point ---

V(1): 12 voltage
 V(3): -0.119999 voltage
 V(2): 1.20119e-006 voltage
 V(n001): 11999.8 voltage
 V(4): -0.119999 voltage
 I(C2): 1.19999e-016 device_current
 I(C1): -1.2e-021 device_current
 I(R4): -0.119998 device_current
 I(R3): -0.00012 device_current
 I(R2): 1.19999e-016 device_current
 I(R1): -0.00012 device_current
 I(V1): -0.00012 device_current
 Ix(u1:3): 0.00012 subckt_current
 Ix(u2:3): -0.119998 subckt_current

Clear(s, Vb, R1, R2, R3, R4, C1, C2) = 1


— E Source —

Example

E1	1	0	4	5	0.5
R1	1	2	8		
R2	2	3	6		
V1	3	0	120		
R3	2	4	2		
R4	4	5	4		
V2	5	0	60		

Note

for commercial use ...

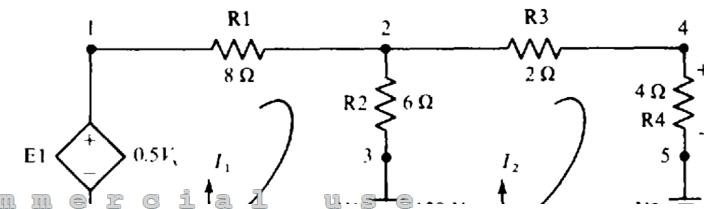

$O := \text{".DC V1 120 120 0.1"}$

$O := \text{".op"}$

$[A \ B \ X \ V \ I] := \text{MNA}(\text{"X"})$

?

Different node convention?

$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ I_E1 \\ I_V1 \\ I_V2 \end{bmatrix}$$

$$V = \begin{bmatrix} 38.18 \\ 38.18 \\ 120 \\ 10.91 \\ 60 \\ 25.91 \\ -13.64 \\ -12.27 \end{bmatrix}$$


$$\begin{aligned} \text{Spice}(\text{"X"}, O, \text{"V(1)"}) &= [0 \ 2] \\ \text{Spice}(\text{"X"}, O, \text{"V(2)"}) &= [0 \ 66] \\ \text{Spice}(\text{"X"}, O, \text{"V(4)"}) &= [0 \ 64] \\ \text{Spice}(\text{"X"}, O, \text{"I(R1)"}) &= [0 \ -8] \\ \text{Spice}(\text{"X"}, O, \text{"I(R4)"}) &= [0 \ 1] \end{aligned}$$

SMa determinants can't handle units:

$M\text{Inverse}(A\#) := \text{maple}(\text{inverse}(A\#))$

— Controlled Sources with Feedback

Controlled Sources with Feedback

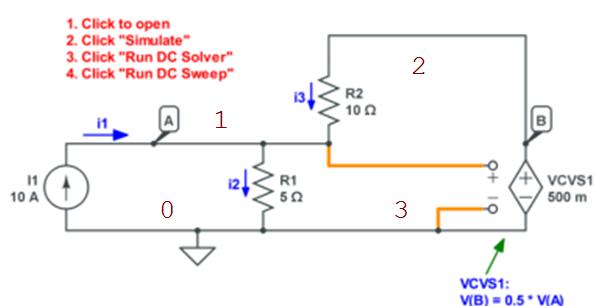

R 0 1 5Ω
R 1 2 10Ω
I 0 1 10A
E 1 2 0 0 0.5

$X := 1$

R1 0 1 5
R2 1 2 10
I1 0 1 10
E2 2 1 0 0 0.5

$X' := 1$

$[A \ B \ X \ V \ I] := \text{MNA}(\text{"X"})$


$$V = \begin{bmatrix} 40 \\ 20 \end{bmatrix} V$$

$$\text{Spice} \left(\text{"X"}, O, \text{".OP"}, \begin{bmatrix} \text{"V(1)"} \\ \text{"V(2)"} \\ \text{"I(R1)"} \end{bmatrix} \right) = \begin{bmatrix} 0 & 50 \\ 0 & 50 \\ 0 & -10 \end{bmatrix}$$

$$I = [-2] A$$

— E: VCVS

Voltage Controlled Voltage Source (VCVS)

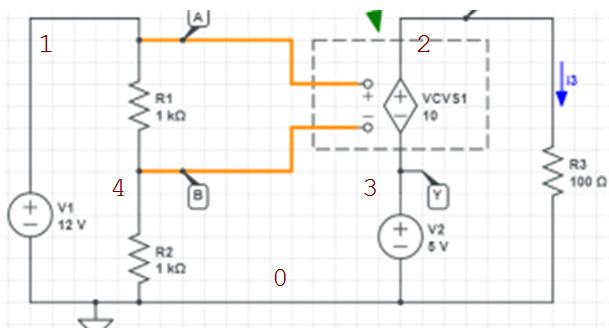


V1 1 0 12V
V2 3 0 5V
R 1 4 1kΩ
R 0 4 1kΩ
R 0 2 100Ω
E 1 2 3 4 10

$X := 1$

V1 1 0 12
V2 3 0 5
R1 1 4 1k
R2 0 4 1k
R3 0 2 100
E1 1 2 3 4 10

$X' := 1$

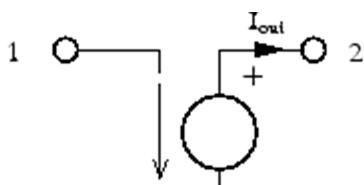$[A \ B \ X \ V \ I] := \text{MNA}(\text{"X"})$



$$V = \begin{bmatrix} 12 \\ 65 \\ 5 \\ 6 \end{bmatrix} V$$


$$\text{Spice} \left(\text{"X"}, O, \text{".OP"}, \begin{bmatrix} \text{"V(1)"} \\ \text{"V(2)"} \\ \text{"V(3)"} \\ \text{"V(4)"} \end{bmatrix}, \begin{bmatrix} \text{"I(R1)"} \end{bmatrix} \right) = \begin{bmatrix} 0 & 12 \\ 0 & 22 \\ 0 & 5 \\ 0 & 6 \\ 0 & 0.01 \end{bmatrix}$$

$$X[5..7] = \begin{bmatrix} I_{V1} \\ I_{V2} \\ I_E \end{bmatrix} \quad |A| = 0 \text{ s}$$

$$I = \begin{bmatrix} -6 \\ -650 \\ 650 \end{bmatrix} \text{ mA}$$

□—G: cccs

Current Controlled Current Source (CCCS)

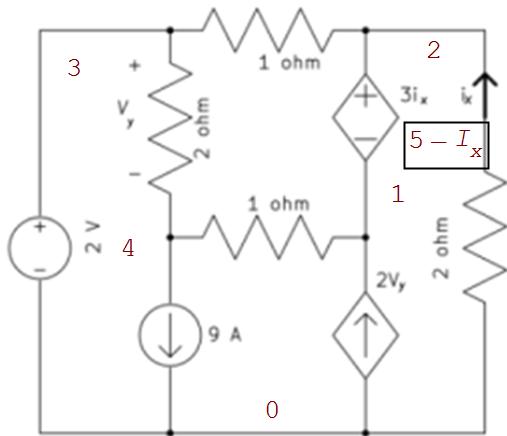


I 4 0 9A
V 3 0 2V
R 1 4 1Ω
R 3 4 2Ω
R 2 3 1Ω
R 0 5 2Ω
Hx 5 2 1 2 3Ω
Gy 3 0 1 4 2S

$\chi := 1$

$$[A \ B \ X \ V \ I] := MNA("X")$$

$$V = \begin{bmatrix} 5 \\ 2 \\ 2 \\ -2 \\ 2 \end{bmatrix} \text{ V}$$
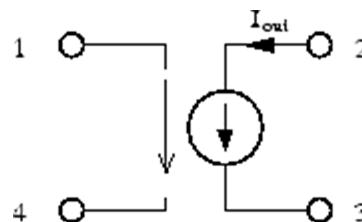
$$I = \begin{bmatrix} -2 \\ -1 \\ 1 \\ 8 \end{bmatrix} \text{ A}$$




$$X[6..9] = \begin{bmatrix} I_{V1} \\ I_{in_Hx} \\ I_{out_Hx} \\ I_{Gy} \end{bmatrix}$$

$$|A| = 4.25 \text{ s}$$

□—F: cccs

Current Controlled Current Source (CCCS)

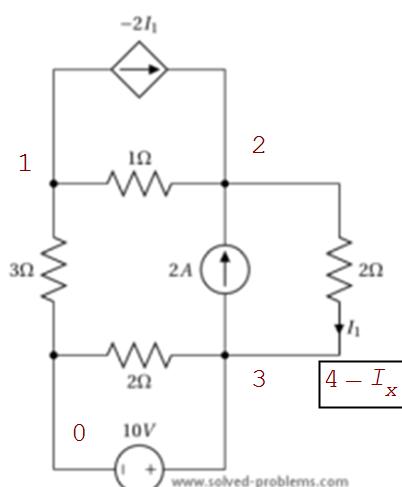

I 3 2 2A
V 3 0 10V
R 0 3 2Ω
R 0 1 3Ω
R 2 4 2Ω
R 1 2 1Ω
Fx 4 1 2 3 -2

$\chi := 1$


$$[A \ B \ X \ V \ I] := MNA("X")$$

$$V = \begin{bmatrix} 6.75 \\ 9.5 \\ 10 \\ 10 \end{bmatrix} \text{ V}$$

$$I = \begin{bmatrix} -7.25 \\ 0.5 \end{bmatrix} \text{ A}$$

LOS VOLTAJES ESTÁN BIEN, CHEKAR LAS CORRIENTES.


$$\frac{|A|}{2} = -0.67 \text{ s}$$

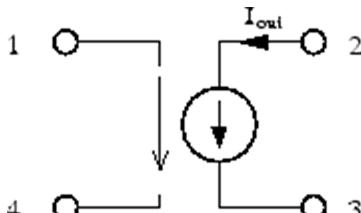

$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ I_V \\ I_Fx \end{bmatrix}$$

□—H: ccvs

Current Controlled Voltage Source (CCVS)

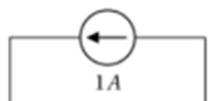

Note


I 0 2 1A
I 0 1 2A
R 0 2 4Ω
R 0 1 3Ω

comenzar con [4.71] al

$$[A \ B \ X \ V \ I] := MNA("X")$$


8 / 9

$$usen [-0.43] \text{ s}$$

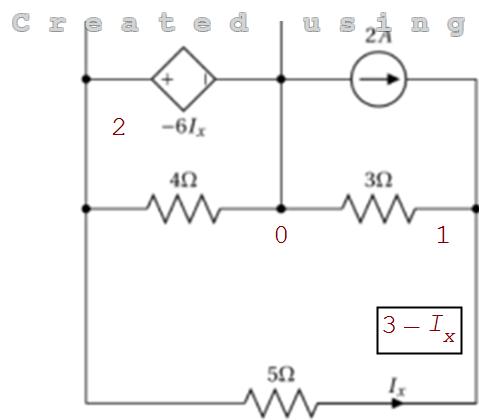

a) $\begin{bmatrix} f & r & e & e \\ R & 2 & 3 & 5\Omega \\ H & 3 & 2 & 0 & 1 & -6\Omega \end{bmatrix} \quad V = \begin{bmatrix} s_1 \\ 2.57 \\ 4.71 \end{bmatrix}$

$$\chi := 1$$

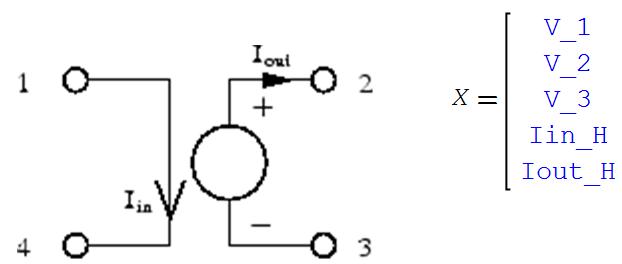

$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_{in_H} \\ I_{out_H} \end{bmatrix}$$

Alvaro

appVersion(4) = "1.2.9018.0"